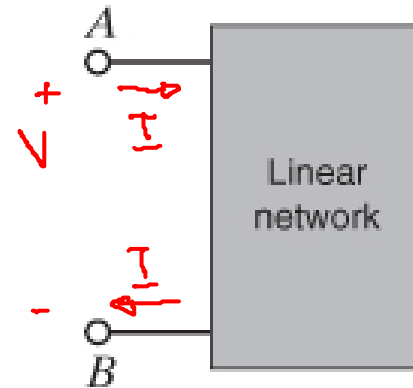


# Two-Port Networks (I&N Chap 16.1-6)

- Introduction
- Impedance/Admittance Parameters
- Hybrid Parameters
- Transmission Parameters
- Interconnecting Two-Port Networks

# Single-Port Circuit

A “port” refers to a pair of terminals through which a single current flows and across which there is a single voltage.




Externally, either voltage or current could be independently specified while the other quantity would be computed. The Thevenin equivalent permits a simple model of the linear network, regardless of the number of components in the network.

# Two-Port

A two-port network requires two terminal pairs (total 4 terminals). Amongst the two voltages and two currents shown, generally two can be independently specified (externally).

How many distinct pairs of independent quantities are possible?




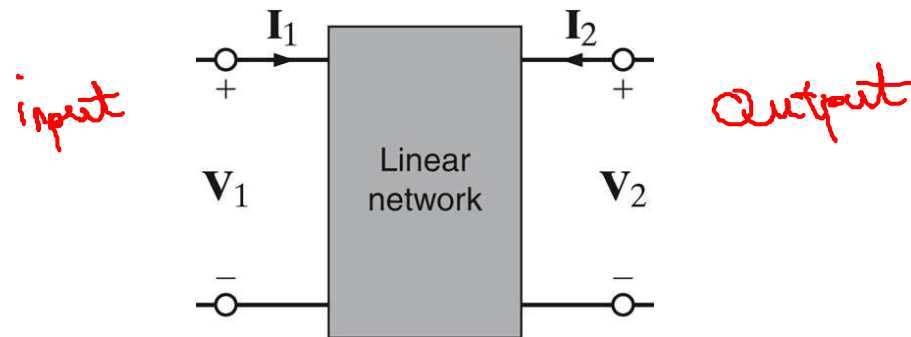
$$C_4^2 = \binom{4}{2} = \frac{4!}{2!(4-2)!} = \frac{24}{2 \times 2} = 6$$




By convention, regard Port 1 as the input and Port 2 as the input (and use the polarity labels shown). We consider circuits with no internal independent sources.

# Motivating Examples

We've seen two-ports before.

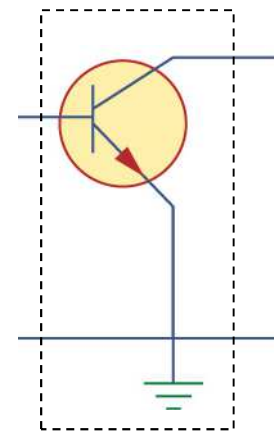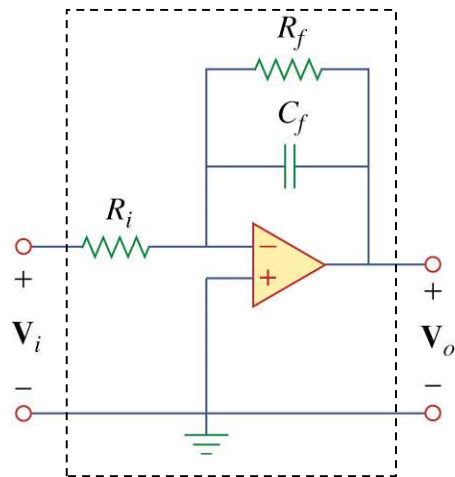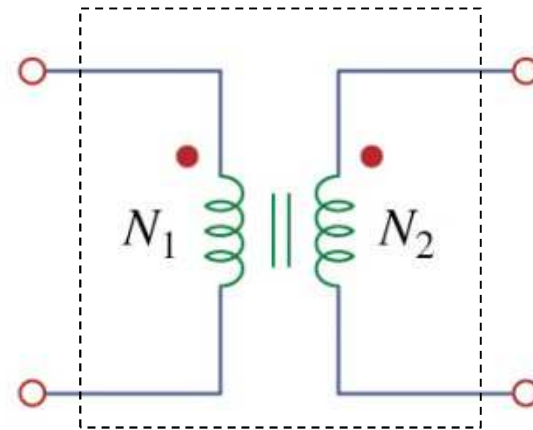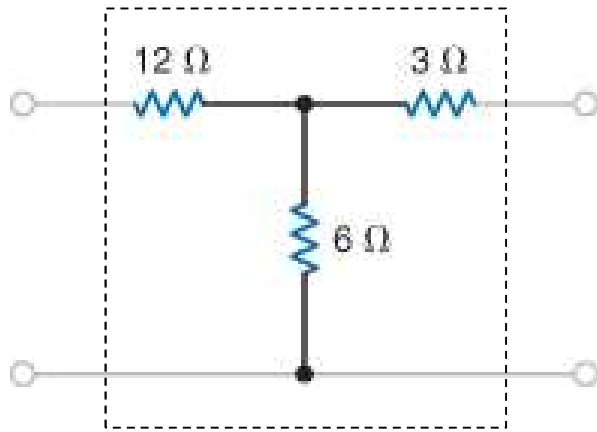

# Admittance Parameters

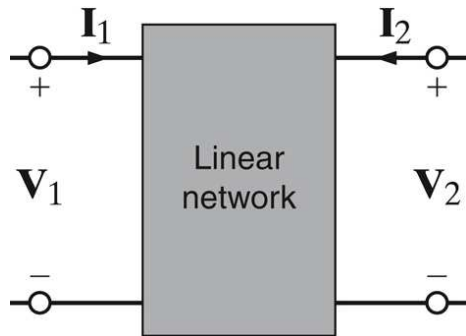

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

only external independent sources!

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

How to determine  $y$  parameters:

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \rightarrow \text{short circuit input admittance}$$


$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \rightarrow \text{short circuit output admittance}$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

transadmittances  
(transfer admittances)

# Impedance Parameters

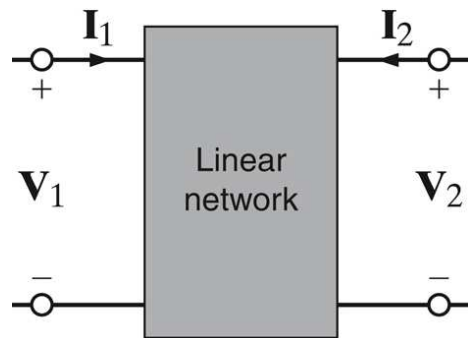

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

*independent sources*

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Determine 2 parameters:

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

*→ open circuit input impedance*

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

*→ O.C. output impedance*

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

*→ transimpedances*

*(transfer impedances)*


$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

*Note: passive components →  $Z_{12} = Z_{21}$*

*$Y_{12} = Y_{21}$  → circuit is "reciprocal"*
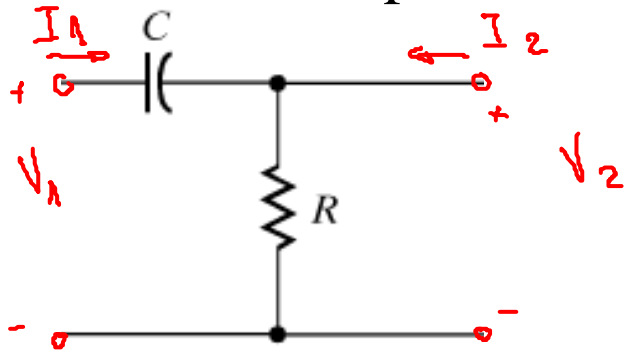
# Example

Find the two-port admittance and impedance parameters.



$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = sC ; \quad y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{1}{R} + sC$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -sC ; \quad y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -sC$$


$$[Y] = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} sC & -sC \\ -sC & \frac{1}{R} + sC \end{bmatrix}$$

$$V_1 = z_{11} I_1 + z_{12} I_2 \Rightarrow z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = R + \frac{1}{sC} \quad ; \quad z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = R = z_{21}$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \Rightarrow z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = R$$

$$[Z] = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} R + \frac{1}{sC} & R \\ R & R \end{bmatrix} ; \quad [Z]^{-1} = [Y] = \begin{bmatrix} R & -R \\ -R & R + \frac{1}{sC} \end{bmatrix} \times \frac{1}{R^2 + R/sC - R^2}$$

# Hybrid Parameters

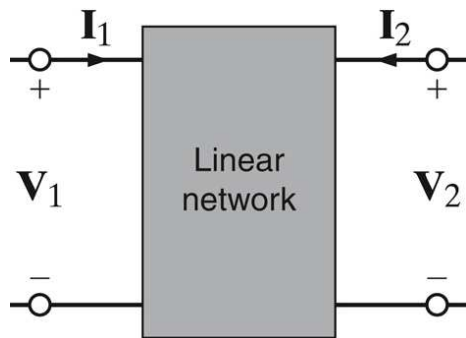

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$h_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \text{s.c. (short circuit) input impedance}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} = \text{o.c. (open circuit) output admittance}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \text{ (s.c. forward current gain)}; \quad h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \text{ (o.c. reverse voltage gain)}$$

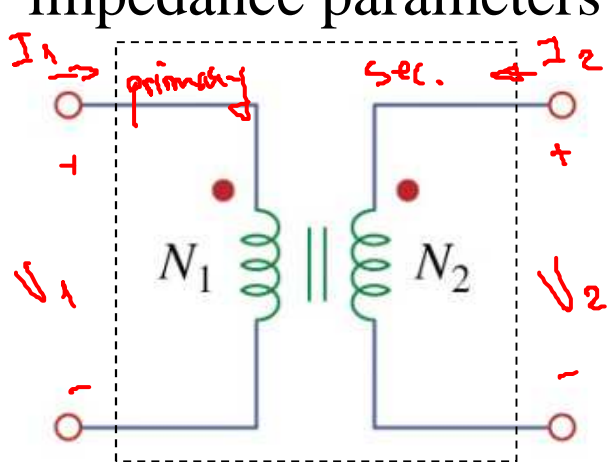E.g. Consider the ideal Xformer. Do the admittance or impedance parameters exist?




$$n = \frac{N_2}{N_1} = \frac{V_2}{V_1} = -\frac{I_1}{I_2}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 & n \\ -\frac{1}{n} & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


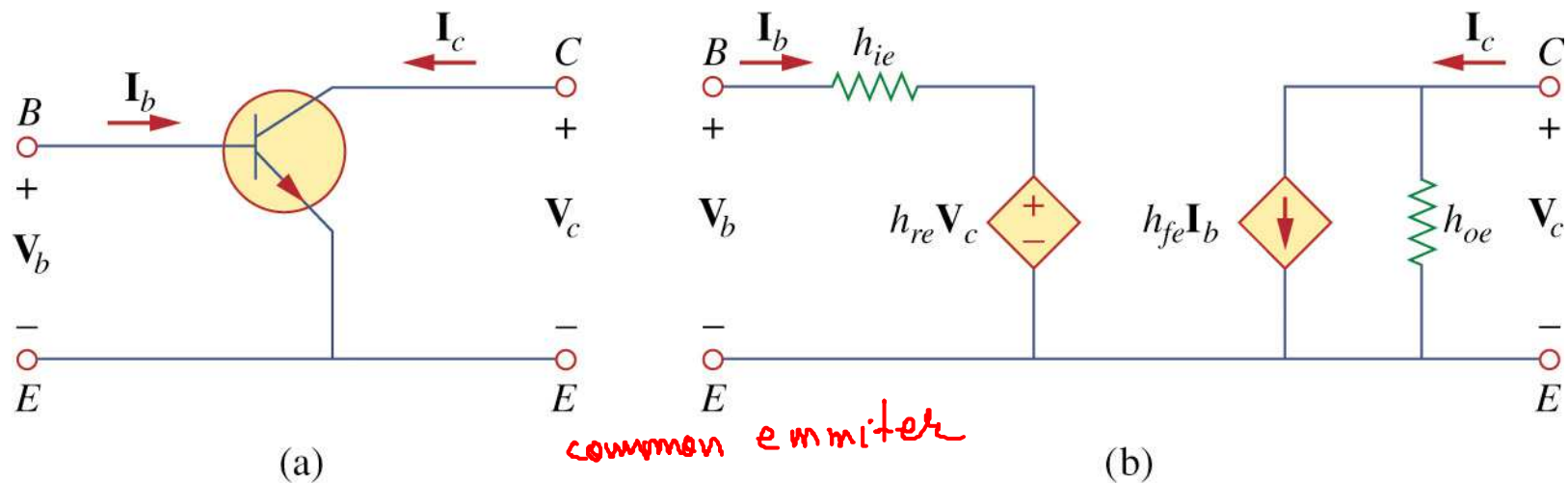
# Transistor Hybrid Parameters

The “small signal” analysis (DC analysis of quiescent point is separate) of BJTs often utilises hybrid parameters.




*common emitter*

$$V_b = h_{ie} I_b + h_{re} V_c$$

$$I_c = h_{fe} I_b + h_{oe} V_c$$

$h_{ie}$  = base input impedance ( $h_{ii}$ )  
 $h_{re} = \frac{V_b}{V_c} \Big|_{I_b=0}$  = reverse voltage feedback ratio  
 $h_{fe}$  = forward current gain (base to collector)  
 $h_{oe} =$

# Transmission Parameters

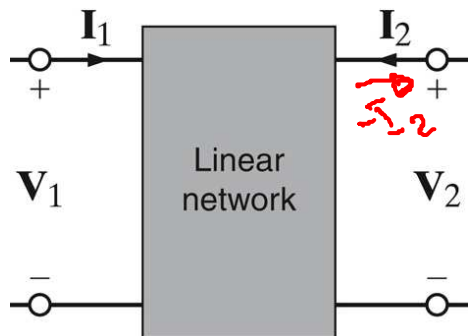


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

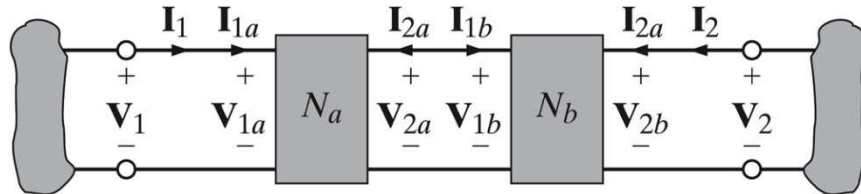Transmission parameters are useful for cascaded networks.



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$= [T_a][T_b] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$[T] = [T_a][T_b] \quad \text{- order is important!}$$

# Parameter Conversions

**TABLE 16.1** Two-port parameter conversion formulas

$[Z]$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$$

$$\begin{bmatrix} \frac{y_{22}}{\Delta_Y} & \frac{-y_{12}}{\Delta_Y} \\ \frac{-y_{21}}{\Delta_Y} & \frac{y_{11}}{\Delta_Y} \end{bmatrix}$$

$$\begin{bmatrix} \frac{A}{C} & \frac{\Delta_T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$$

$$\begin{bmatrix} \frac{\Delta_H}{h_{22}} & \frac{h_{12}}{h_{22}} \\ \frac{-h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$$

$[Y]$

$$\begin{bmatrix} \frac{z_{22}}{\Delta_Z} & \frac{-z_{12}}{\Delta_Z} \\ \frac{-z_{21}}{\Delta_Z} & \frac{z_{11}}{\Delta_Z} \end{bmatrix}$$

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

$$\begin{bmatrix} \frac{D}{B} & \frac{-\Delta_T}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$$

$$\begin{bmatrix} \frac{1}{h_{11}} & \frac{-h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta_H}{h_{11}} \end{bmatrix}$$

$[T]$

$$\begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta_Z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix}$$

$$\begin{bmatrix} \frac{-y_{22}}{y_{21}} & \frac{-1}{y_{21}} \\ \frac{y_{21}}{y_{21}} & \frac{y_{21}}{y_{21}} \\ \frac{-\Delta_Y}{y_{21}} & \frac{-y_{11}}{y_{21}} \\ \frac{y_{21}}{y_{21}} & \frac{y_{21}}{y_{21}} \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\begin{bmatrix} \frac{-\Delta_H}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{h_{21}}{h_{21}} & \frac{h_{21}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \\ \frac{h_{21}}{h_{21}} & \frac{h_{21}}{h_{21}} \end{bmatrix}$$

$[h]$

$$\begin{bmatrix} \frac{\Delta_Z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ \frac{-z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix}$$


$$\begin{bmatrix} \frac{1}{y_{11}} & \frac{-y_{12}}{y_{11}} \\ \frac{y_{11}}{y_{11}} & \frac{y_{11}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & \frac{\Delta_Y}{y_{11}} \\ \frac{y_{11}}{y_{11}} & \frac{y_{11}}{y_{11}} \end{bmatrix}$$

$$\begin{bmatrix} \frac{B}{D} & \frac{\Delta_T}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{bmatrix}$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$$

# Other 2-Port Interconnections

Parallel

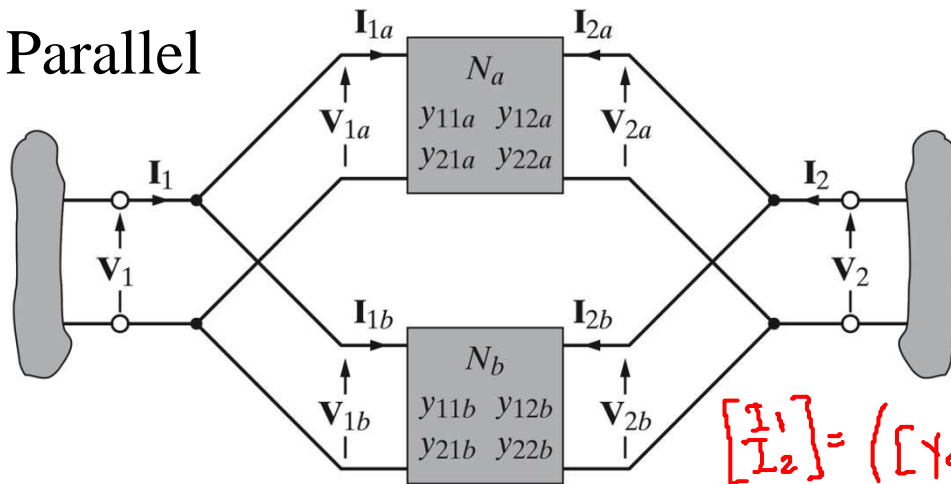


$$V_1 = V_{1a} = V_{1b} ; V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b} ; I_2 = I_{2a} + I_{2b}$$

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = [Y_a] \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} ; \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = [Y_b] \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = ([Y_a] + [Y_b]) \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Series

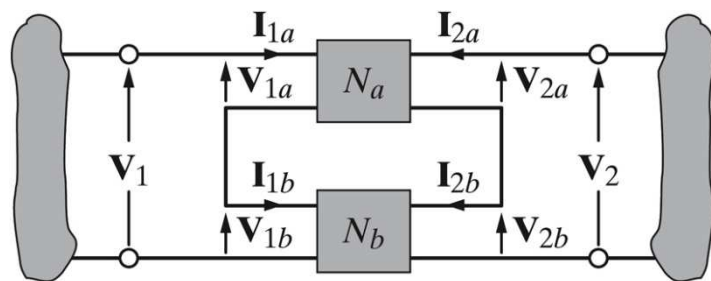

$$I_1 = I_{1a} = I_{1b} ; I_2 = I_{2a} = I_{2b}$$


$$V_1 = V_{1a} + V_{1b} ; V_2 = V_{2a} + V_{2b}$$

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = [Z_a] \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} ; \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = [Z_b] \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$


$$\Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = ([Z_a] + [Z_b]) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$
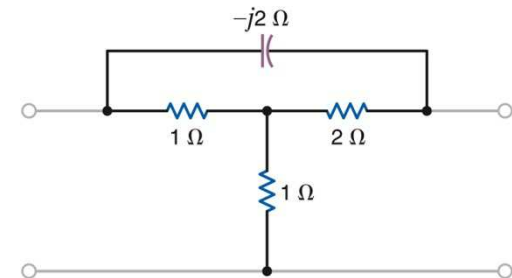
# I&N Examples 16.5 & 16.6

For the circuit shown, use the interconnected parallel and series networks below to find, respectively, the circuit admittance and impedance parameters.




$[y]$  from parallel interconnection

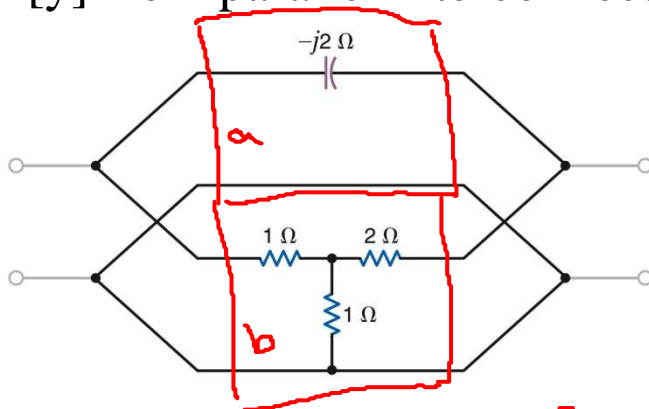

$$[y_a] = \begin{bmatrix} \frac{j}{2} & -\frac{j}{2} \\ -\frac{j}{2} & \frac{j}{2} \end{bmatrix}; [y_b] = \begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix}$$

$$[y] = [y_a] + [y_b] =$$




$[z]$  from series interconnection

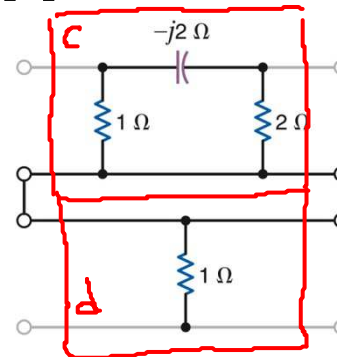

$$[z_c] = \begin{bmatrix} (2-j2) \parallel 1 & z_{12} \\ z_{21} & (1-j2) \parallel 2 \end{bmatrix}$$

$$[z_d] = \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}; [z] = [z_c + z_d]$$

# I&N Example 16.3

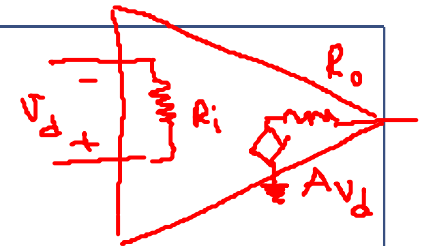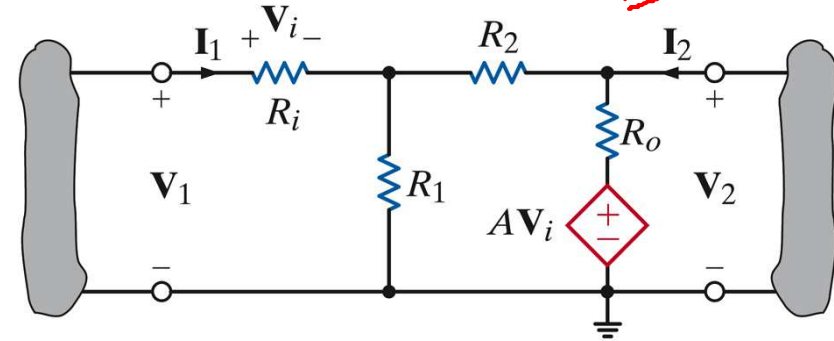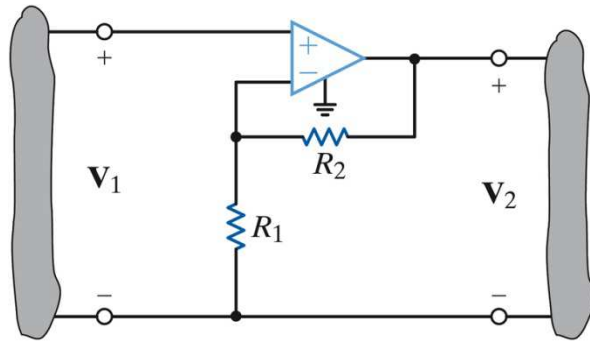

Find the hybrid parameters for the circuit using the non-ideal op-amp model.

ideal op-amp :  $\frac{V_2}{V_1} = 1 + \frac{R_2}{R_1}$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} ; \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} \\ h_{21} \end{bmatrix} I_1 \Big|_{V_2=0} = \begin{bmatrix} R_i + R_1 \parallel R_2 \\ -\left[ \frac{R_1}{R_1 + R_2} + \frac{A R_i}{R_0} \right] \end{bmatrix} I_1 \Big|_{V_2=0}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{12} \\ h_{22} \end{bmatrix} V_2 \Big|_{I_1=0} = \begin{bmatrix} \frac{R_1}{R_1 + R_2} \\ \frac{1}{R_0} + \frac{1}{R_1 + R_2} \end{bmatrix} V_2 \Big|_{I_1=0}$$

$\Rightarrow [h] = \begin{bmatrix} \phantom{0} \\ \phantom{0} \end{bmatrix}$

# I&N Example 16.9

Analyse the effect of load  $R_L$  on the gain and gain error using a non-ideal op-amp model (use  $A=20000$ ,  $R_i=1\text{ M}\Omega$ ,  $R_o=500\ \Omega$ ,  $R_1=1\text{ k}\Omega$  and  $R_2=49\text{ k}\Omega$ ).

ideal op-amps  $\rightarrow \frac{V_2}{V_1} = 50 = A_{ideal}$


$$V_1 = h_{11} I_1 + h_{12} V_2 \quad / \times h_{21}$$

$$- \frac{(I_2 = h_{21} I_1 + h_{22} V_2) / \times h_{11}}$$


$$h_{21} V_1 + \frac{h_{11} V_2}{R_L} = h_{21} h_{12} V_2 - h_{11} h_{22} V_2$$

$$= \Delta h V_2$$
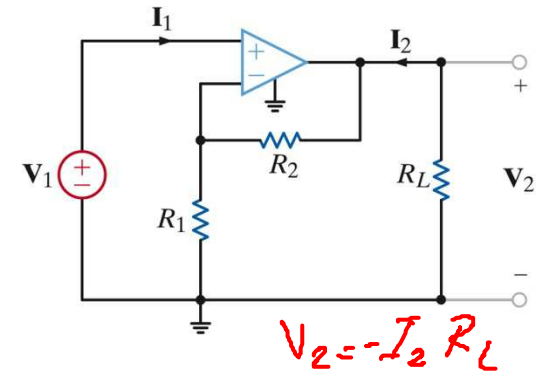
$$\Rightarrow \frac{V_2}{V_1} = - \frac{h_{21}}{\Delta h + \frac{h_{11}}{R_L}} = \frac{49.9}{1 + \frac{1.25}{R_L}} = A_{actual}$$



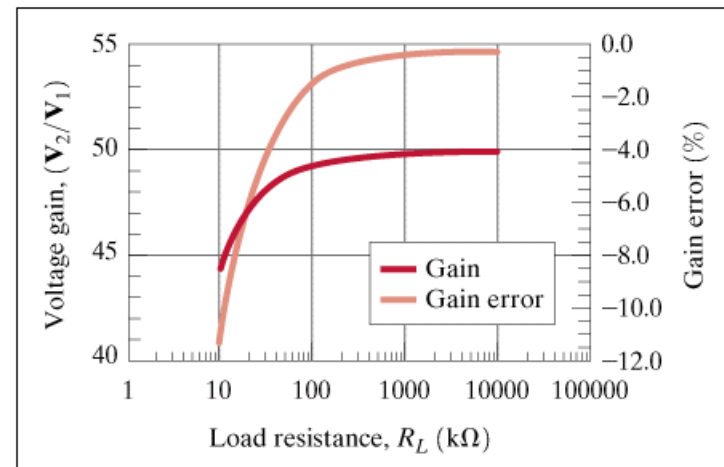
$$\text{Gain error} = \frac{A_{actual} - A_{ideal}}{A_{ideal}}$$


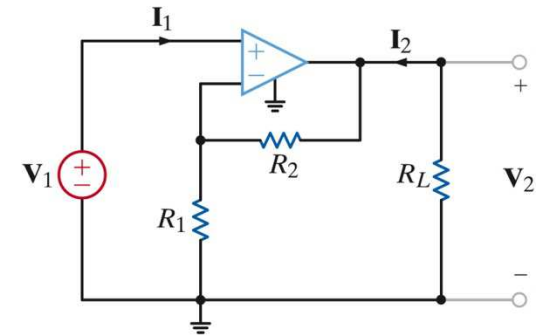
# I&N Example 16.10

Using the op-amp circuit from example 16.9 but using a different value for  $R_2$ , compare the single-stage vs two-stage amplifier to achieve a gain of 10,000.



single stage :  $A_V = 1 + \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = 9,999$

e.g.  $R_1 = 1\text{ k}\Omega \Rightarrow R_2 = 9.999\text{ M}\Omega$

$\Rightarrow [h] = \begin{bmatrix} 1.001\text{ M}\Omega & 1 \times 10^{-4} \\ -4 \times 10^7 & 2.000\text{ ms} \end{bmatrix} \Rightarrow \frac{V_2}{V_1} = \frac{6667}{1 + \frac{166.7}{R_L}}$


problems : 1)  $R_2 > R_1$  (ideally want  $R_1 \rightarrow \infty$ )

2)  $A_{\text{actual}} \approx 6.667 (R_L \rightarrow \infty)$  - same order of magnitude as  $A_{\text{ideal}}$  [want  $A_{\text{open loop}} \rightarrow A_{\text{closed loop}}$ ]

$\Rightarrow$  two stage @  $A = 100$

$R_1 = 1\text{ k}\Omega ; R_2 = 99\text{ k}\Omega$

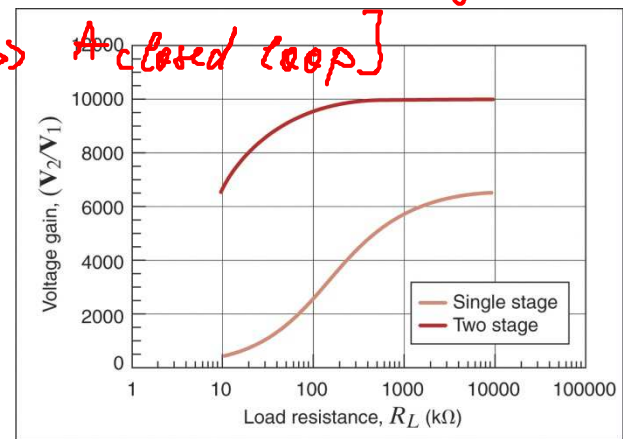$[h] = \begin{bmatrix} 1.001\text{ M}\Omega & 0.01 \\ -4 \times 10^7 & 2\text{ ms} \end{bmatrix} \Rightarrow \frac{V_2}{V_1} = \frac{99.5}{1 + \frac{2.49}{R_L}}$






# Equivalent Circuits from [z]

A reciprocal network with known impedance parameters can be represented by the “T-network” of impedances shown.

$$V_1 = (z_{11} - z_{12}) I_1 + z_{12} (I_1 + I_2)$$

$$= z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{12} I_1 + z_{22} I_2$$

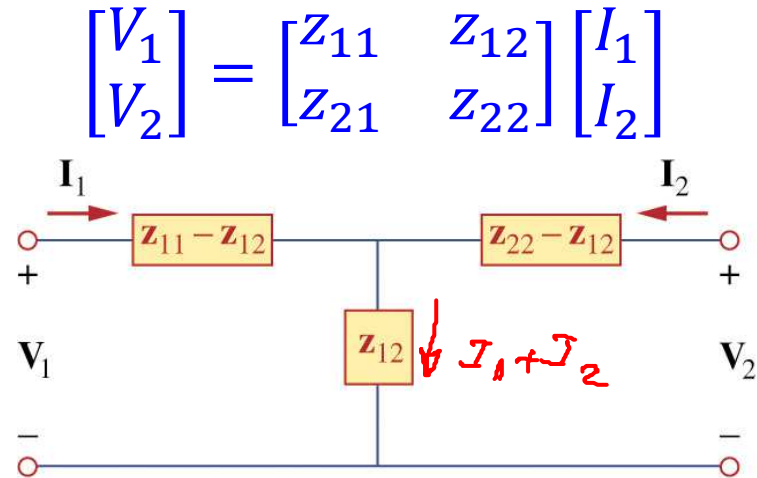

# Summary

- A two-port network has an input port and an output port, each with each port involving a single current and a single voltage.
- If the two-port network is linear and does not contain any independent sources, it may be possible to characterize up to 6 different sets of matrix relationships. We discussed four: admittance [y], impedance [z], hybrid [h], and transmission [T]. If the parameters exist, they can be calculated or measured individually by short-circuiting or open-circuiting the appropriate port.
- A two-port network is reciprocal if  $y_{12}=y_{21}$ ,  $z_{12}=z_{21}$ ,  $h_{12}=-h_{21}$ . If the linear network only contains passive elements, it is reciprocal.
- When two-port networks are connected (a) in series, their impedance parameters add; (b) in parallel, their admittance parameters add; and (c) in cascade, their transmission parameters multiply.